




## Lesson 5



# Thermomechanical Measurements for Energy Systems (MENR)
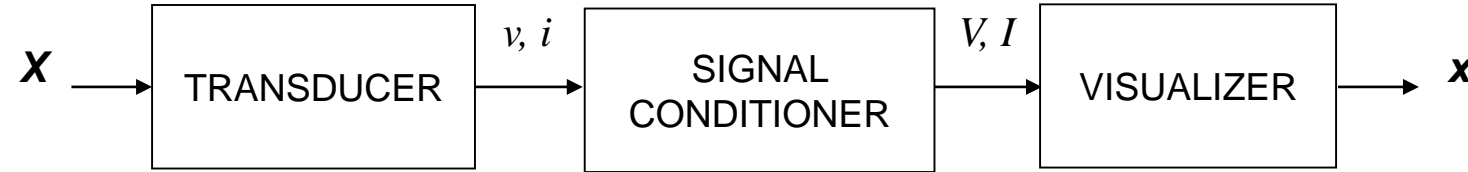
# Measurements for Mechanical Systems and Production (MMER)


We will now analyze more in depth each one of the *functional blocks* of the general **measurement chain** ...



In the industry and in most modern measurement applications, the *measurement chain is electric* and the information passes through the different stages as **voltage signal** or as a **current** !

Despite the enormous technological advancements of the last 30 years, the main electrical visualizer instruments can still be included in only **three** classes:

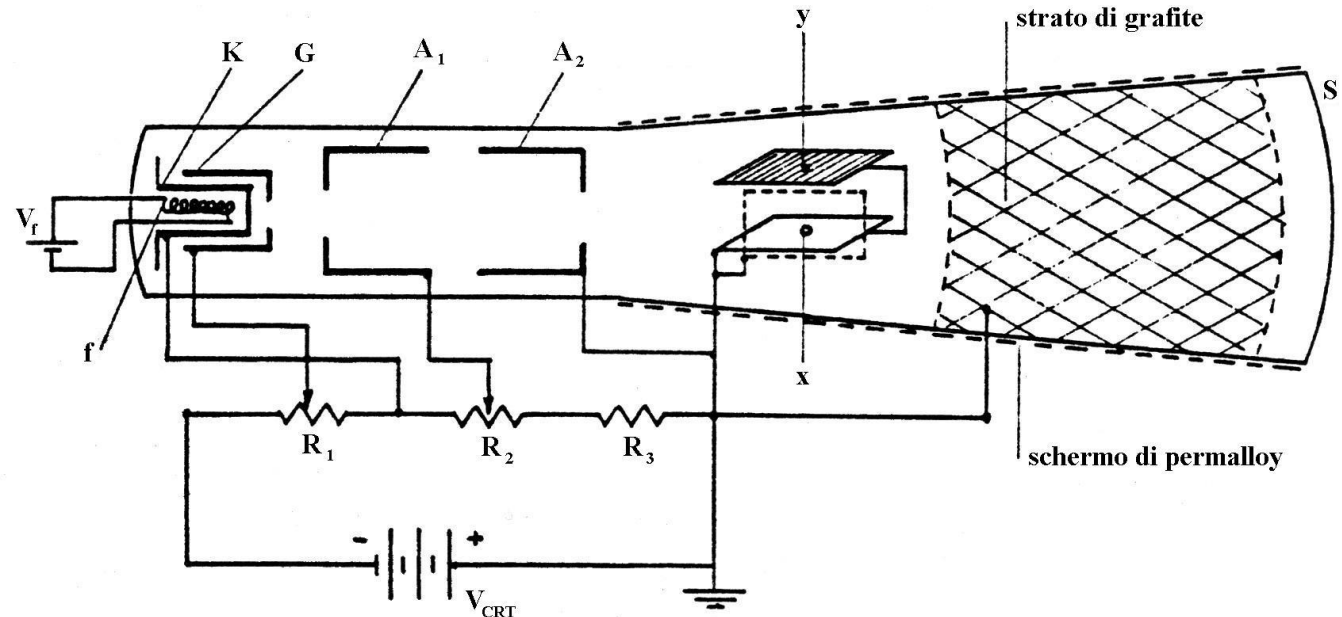1. The **galvanometer**
2. The **oscilloscope**
3. The **digital voltmeter**



**The analog OSCILLOSCOPE →**






**Analog oscilloscope** is the older type and can instantaneously display on the screen the waveform of the input signal !

The *periodic input signal* is combined on the fluorescent screen with an *internal sawtooth (sweep) signal* !


A **trigger** synchronizes the two signals !

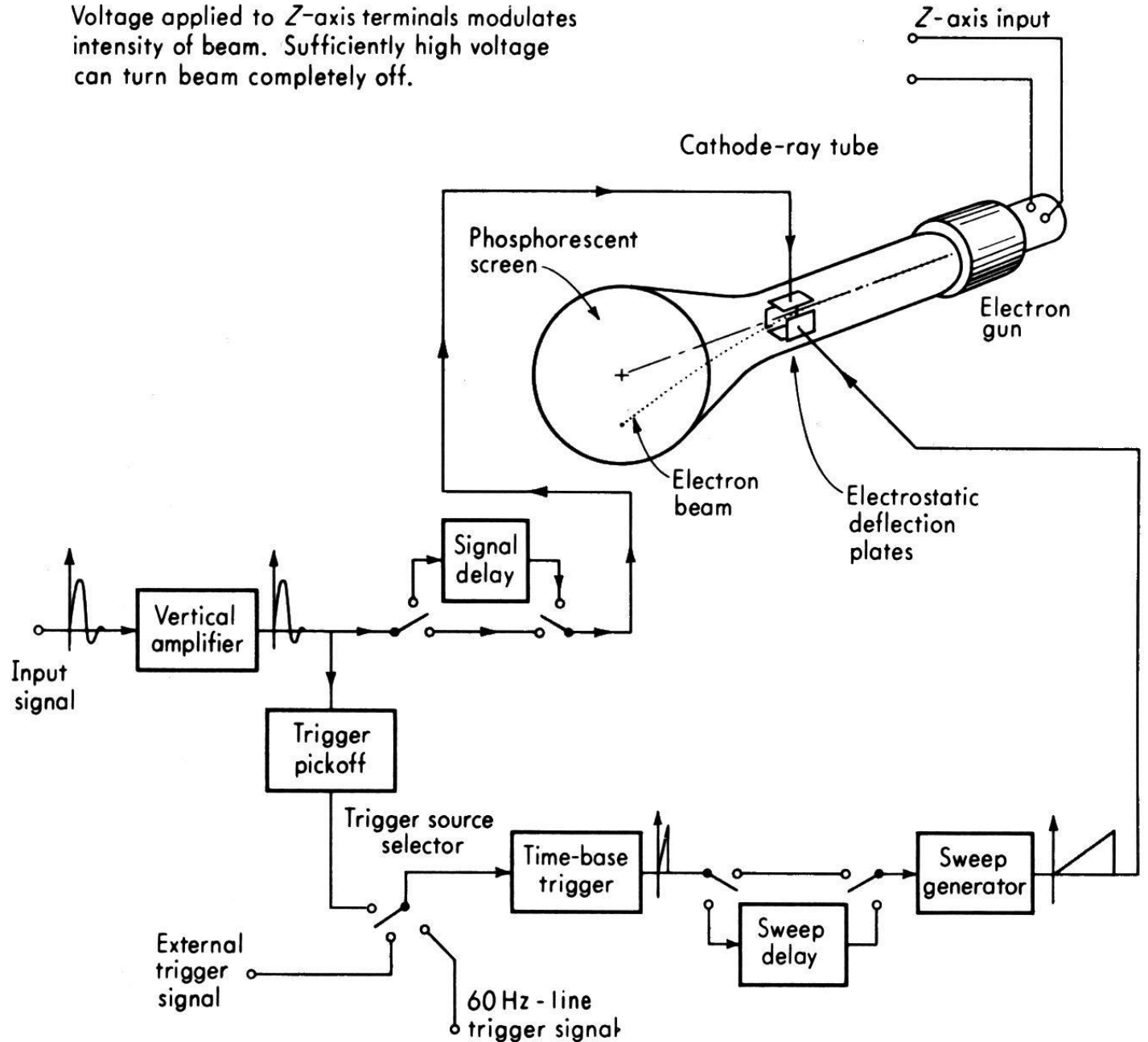Voltage applied to Z-axis terminals modulates intensity of beam. Sufficiently high voltage can turn beam completely off.




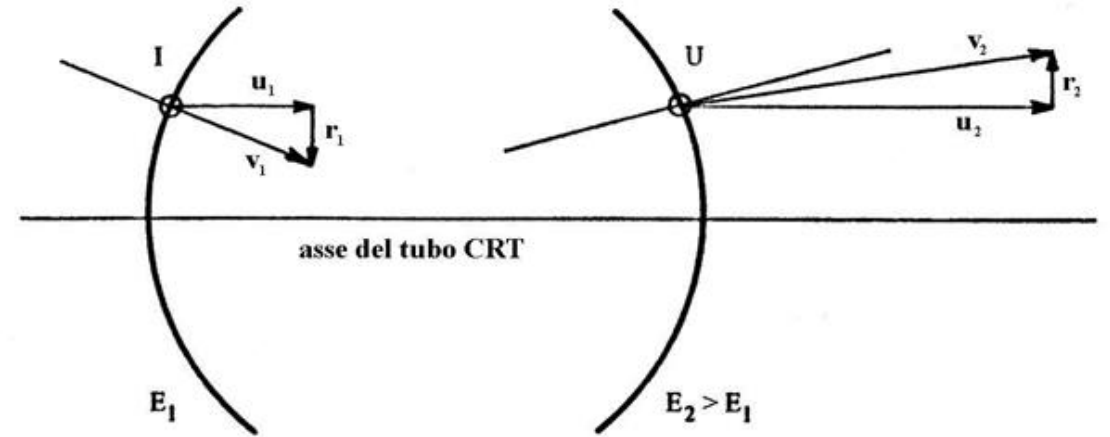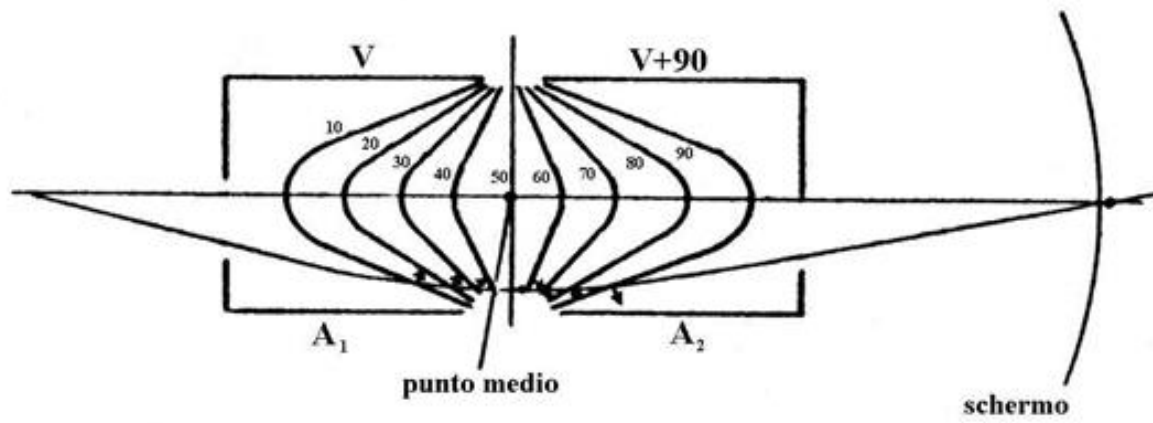


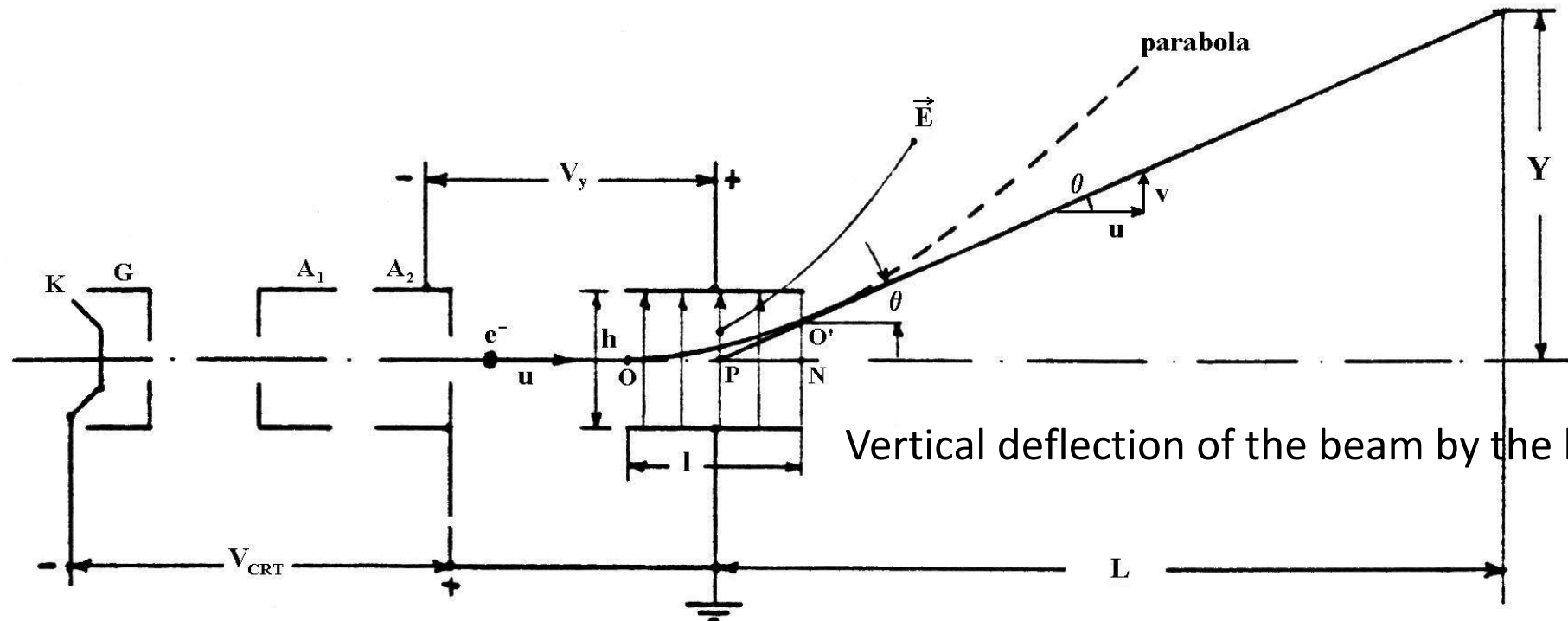
*Acceleration and collimation of the electron beam !*



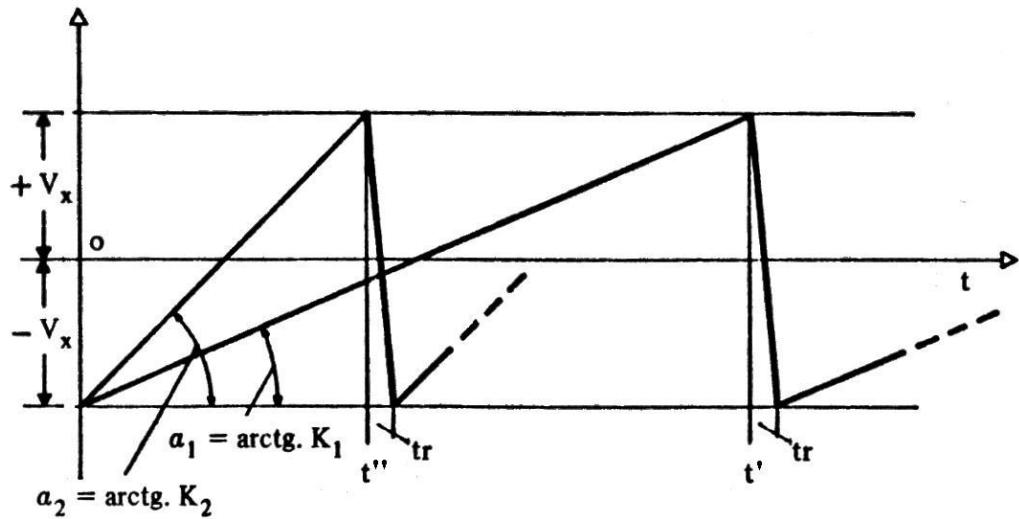Vertical deflection of the beam by the horizontal plates !





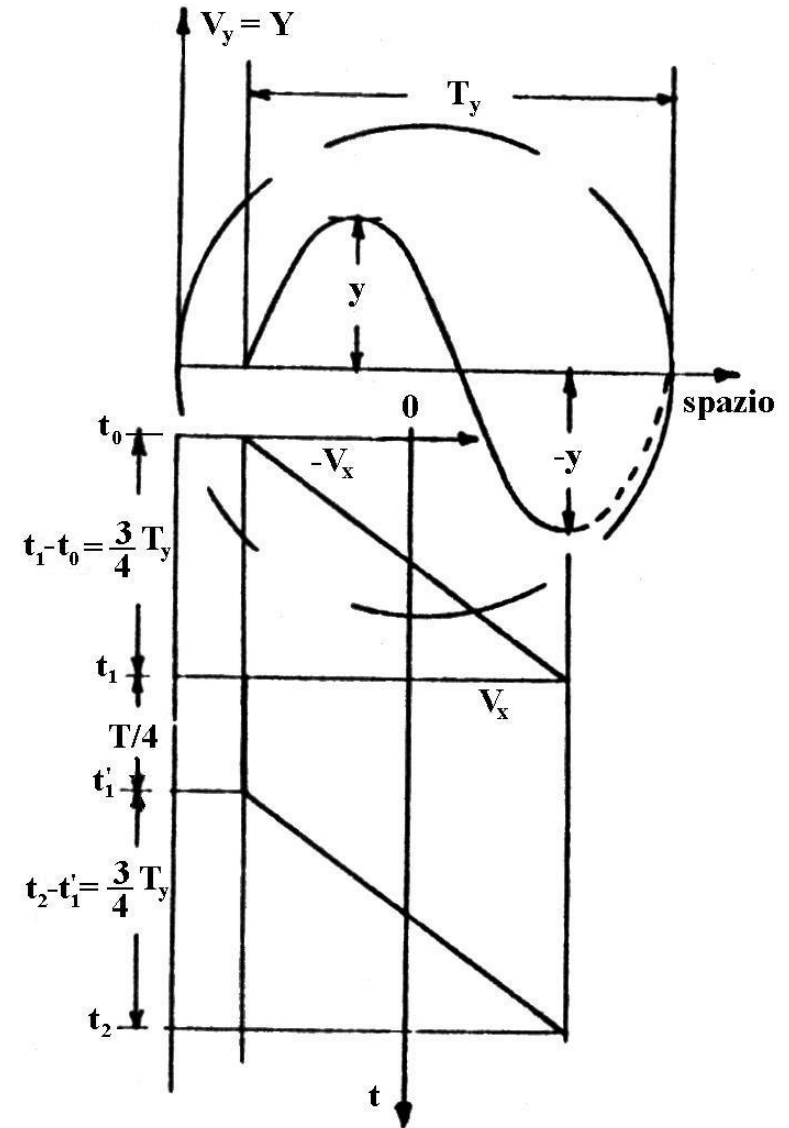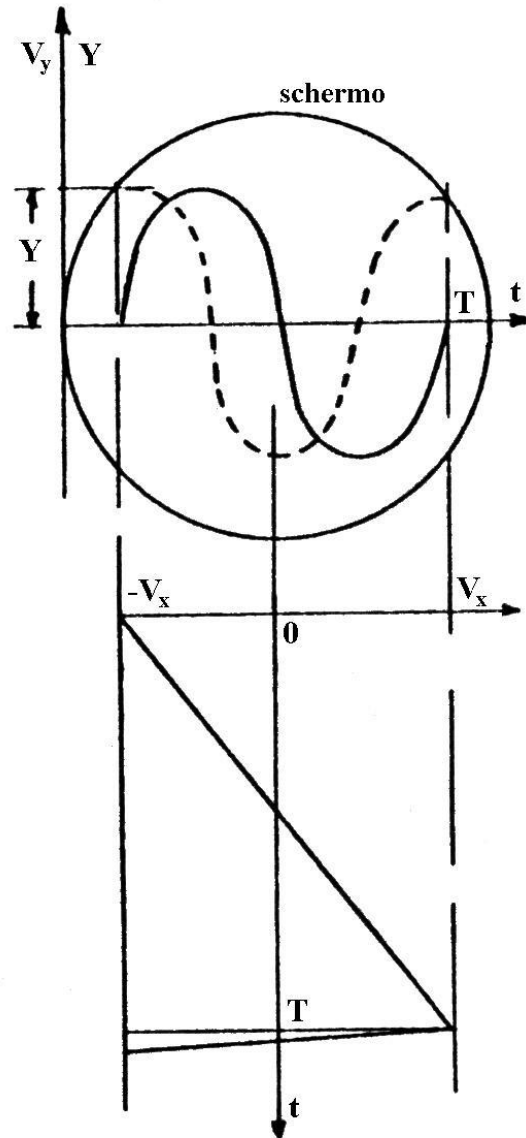*Sawtooth (sweep) and sinusoidal signal combination on the CRT screen !*






# Digital OSCILLOSCOPE ...

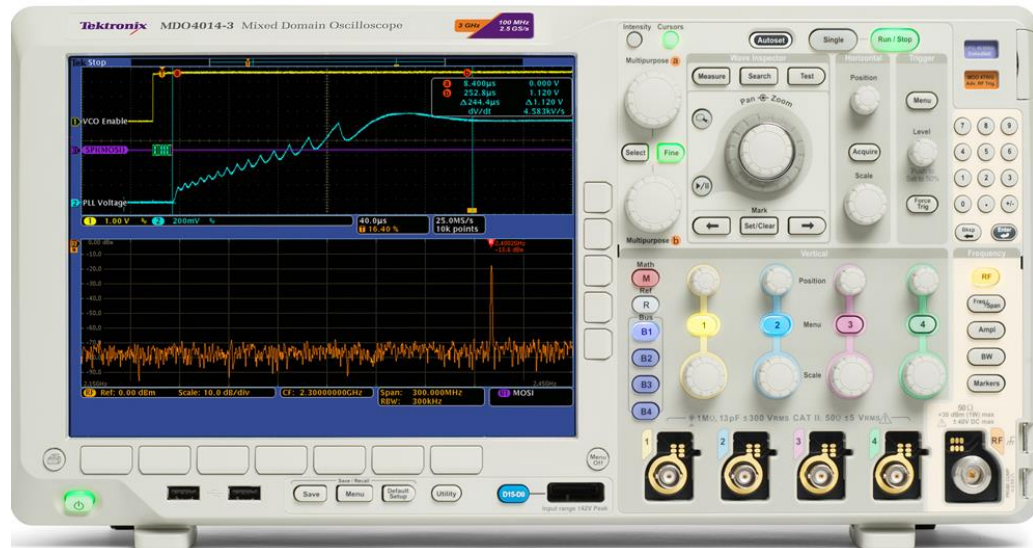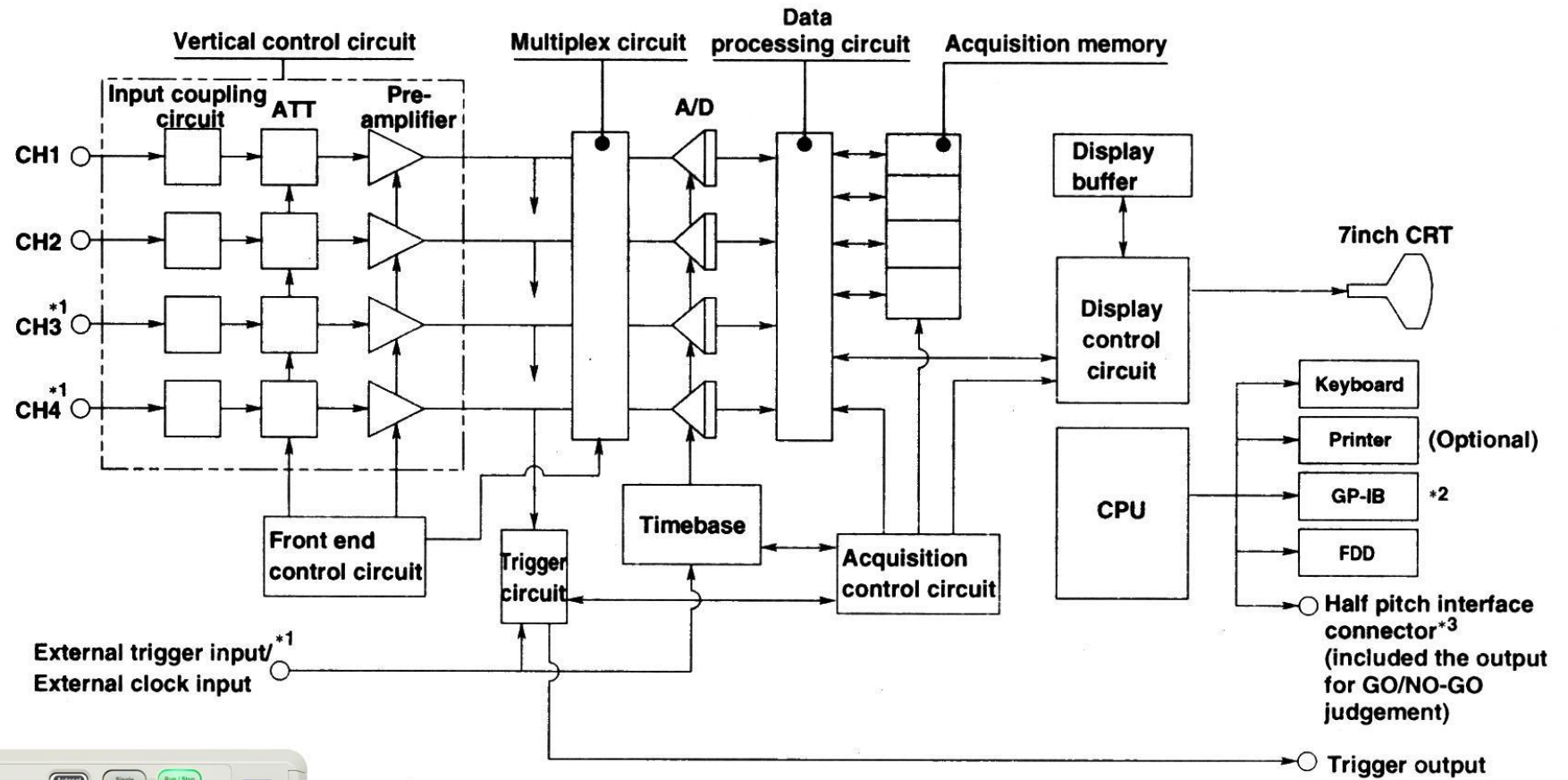



The digital oscilloscope does the same tasks as the *analog* scope (and much more) but it is actually a **digital voltmeter** that samples the input signal and displays it on a VGA screen !

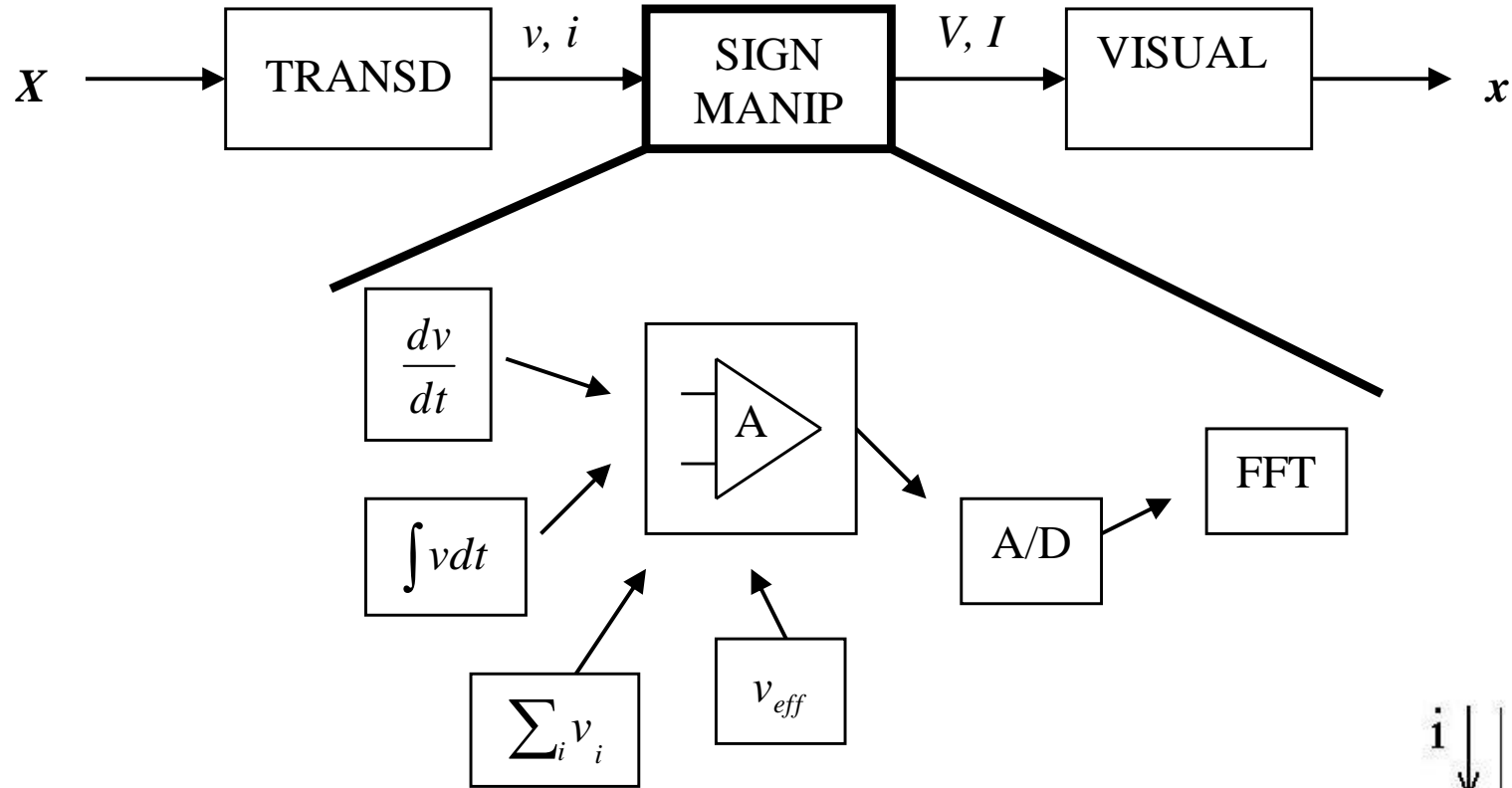We will now study the most important **signal manipulation circuits** used in measurement instruments :





In modern and complex industry measurement system, the signal outputted by the transducer is almost always an *electrical signal v or i* for which, most of the time, we need to enhance the information content (the **intensity of the measurand**) !

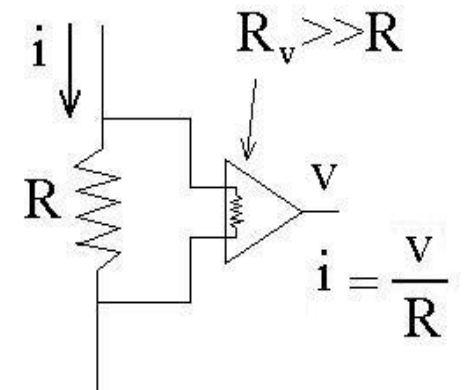
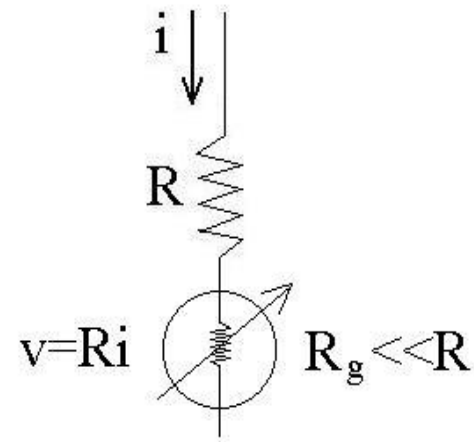
It is always possible to measure a voltage with an amperometer and a current with a voltmeter ...



## The rectifier diode :

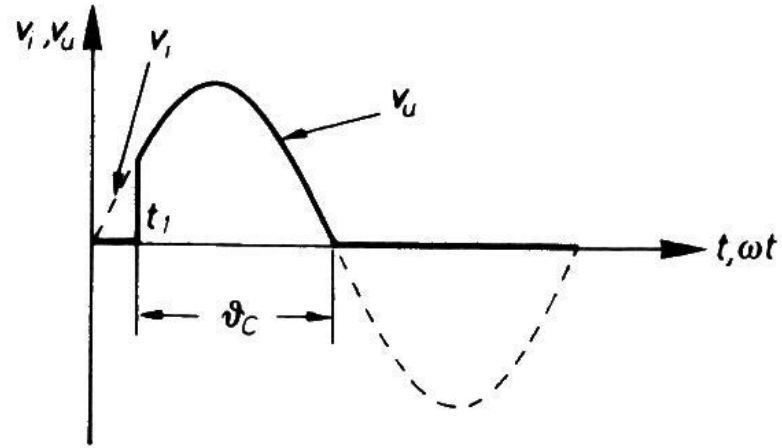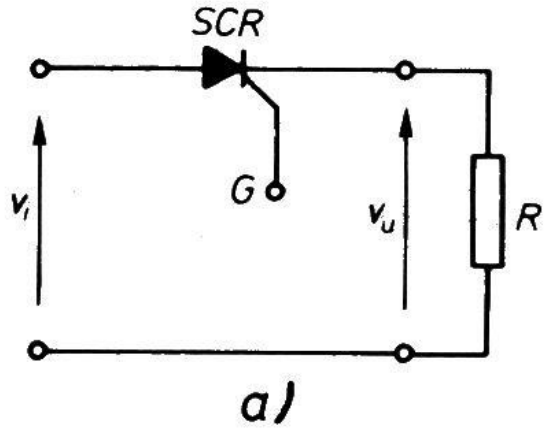

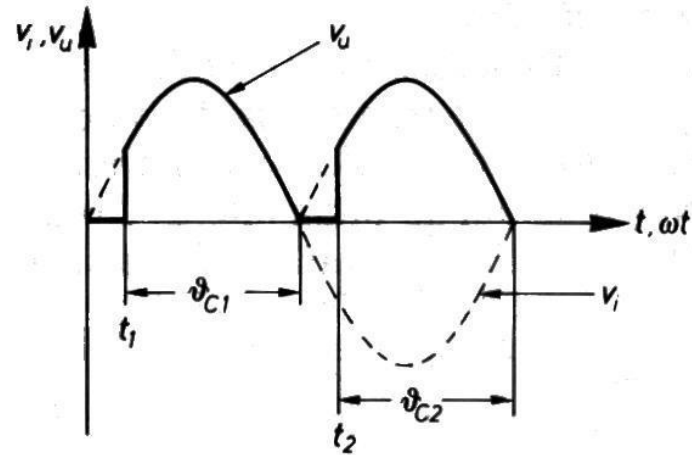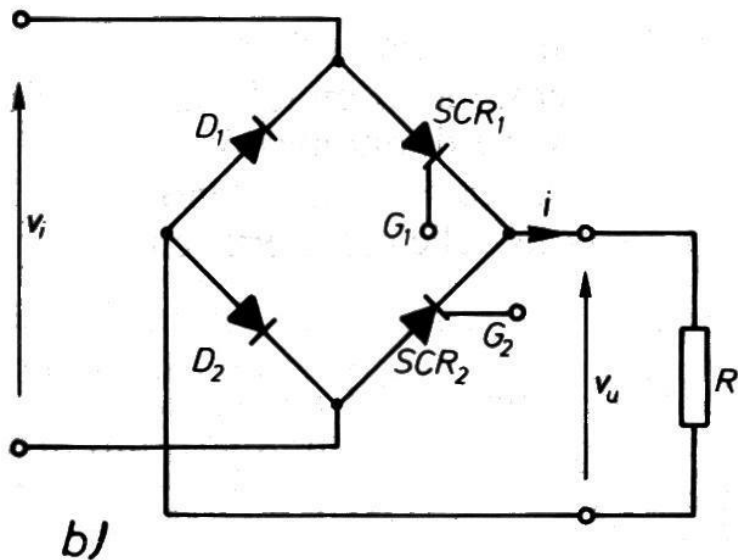
a) The **SCR diode** works here as a half-wave rectifier !



b) The **Gretz bridge** with 4 SCR diodes works here as a full-wave rectifier !



## The low-pass “RC” circuit

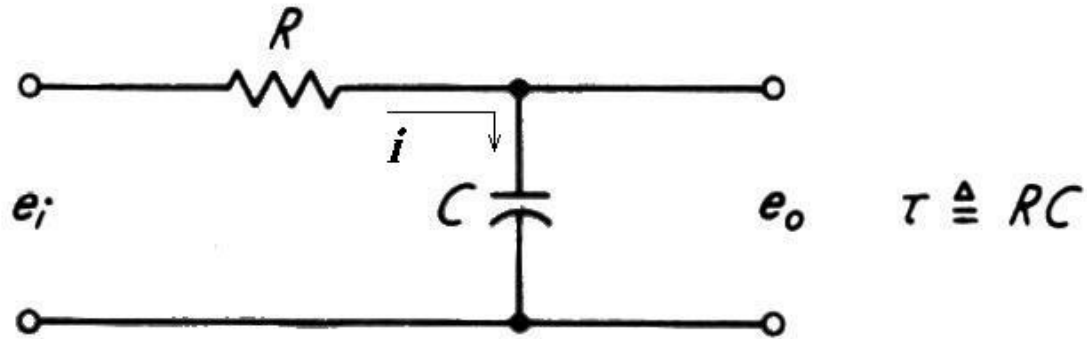

Let's study the *two electric circuits*

input (voltage) signal:  $v_i = (R + X_C) \cdot i$

output (voltage) signal:  $v_o = X_C \cdot i$

the current is  $i = \frac{v_i}{R + X_C}$  and the output voltage:  $v_o = X_C \cdot \frac{v_i}{R + X_C} = \frac{v_i}{\frac{R}{X_C} + 1}$

but  $X_C = \frac{1}{j\omega C}$  is the **capacitive reactance**, therefore the output/input ratio is :  $\frac{v_o}{v_i} = \frac{1}{j\omega RC + 1}$

Considering  $\omega_c = \frac{1}{RC} = \frac{1}{\lambda}$  the output/input ratio is also:

$$\frac{v_o}{v_i} = \frac{1}{j\omega\lambda + 1}$$


We can calculate the modulus of the previous complex function :

$$G = \frac{v_o}{v_i} = \frac{1}{\sqrt{\left(\frac{\omega}{\omega_c}\right)^2 + 1}}$$

the **gain** !

And the phase delay:  $\varphi = \text{arctg}(-\omega\lambda)$

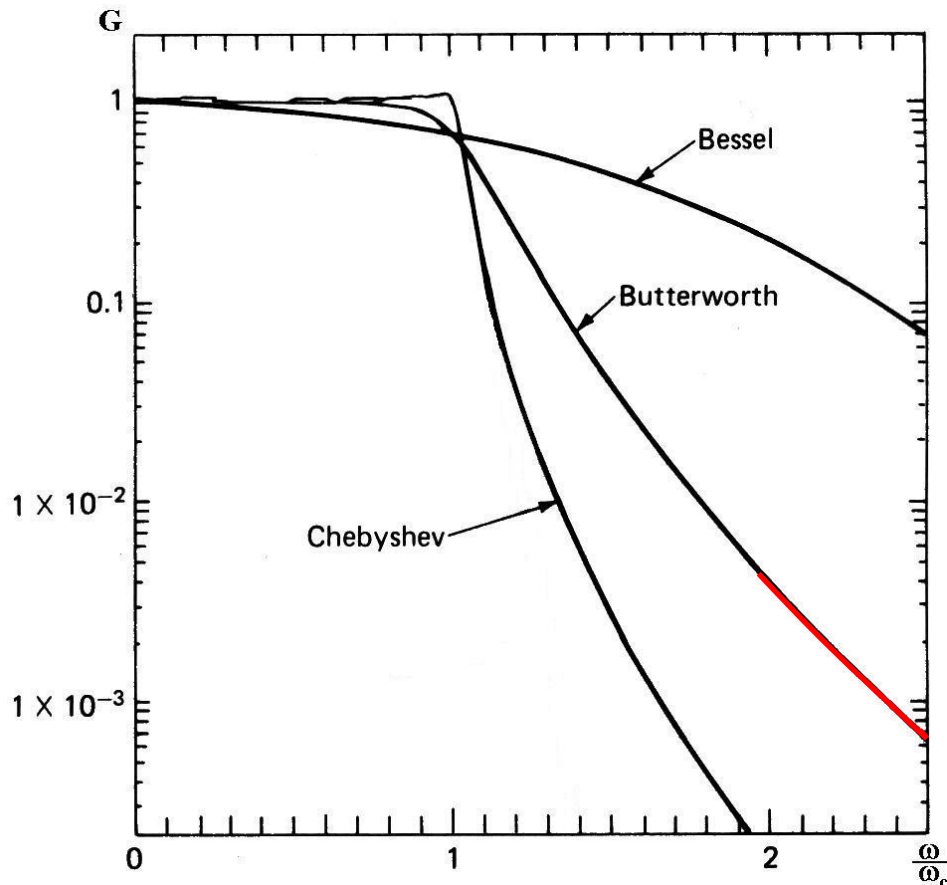We recognize the **frequency response** of a simple **1<sup>st</sup> order electric signal manipulation** stage !



for

$\omega = 0$	$G = 1$
$\omega \rightarrow \infty$	$G = 0$
$\omega = \omega_c$	$G = \frac{1}{\sqrt{2}}$

The RC circuit is a **low-pass filter** (**one pole Butterworth filter**) with a **-3 db cut-off frequency**:


$$f_c = \frac{1}{2\pi RC}$$

Note that for  $|j\omega CR| \gg 1$  which is  $\omega \gg \frac{1}{CR} = \omega_c$

the **output signal** is also the “integral” of the input signal:

$$v_o(t) = \frac{1}{\lambda} \cdot \frac{1}{j\omega} v_i(t)$$

## The high-pass “CR” circuit

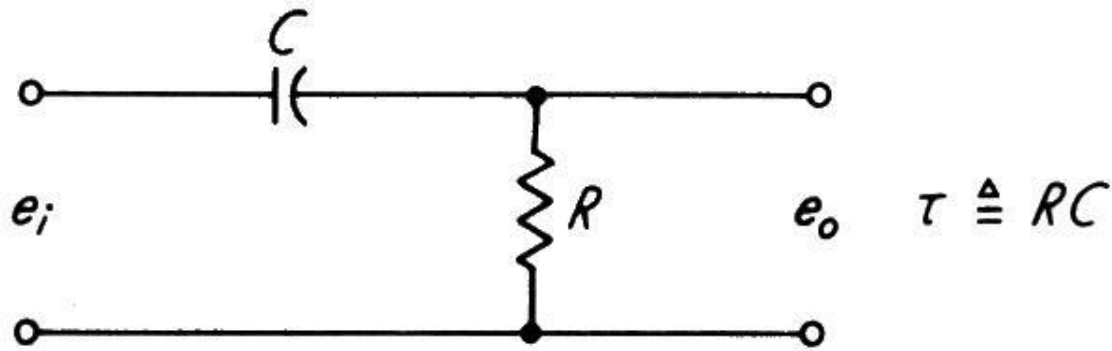

The *two electric circuits* equations now are:

input (voltage) signal:  $v_i = (X_C + R) \cdot i$


output (voltage) signal:  $v_o = R \cdot i$

which now result in :  $v_o = R \cdot \frac{v_i}{X_C + R}$  with the same notations:  $X_C = \frac{1}{j\omega C}$   $\omega_c = \frac{1}{RC} = \frac{1}{\lambda}$

The output/input ratio is :  $\frac{v_o}{v_i} = \frac{R}{X_C + R} = \frac{j\omega CR}{1 + j\omega CR} = \frac{j\omega\lambda}{1 + j\omega\lambda}$

It is also a **1<sup>st</sup> order electric signal manipulation stage** with a **gain** of :
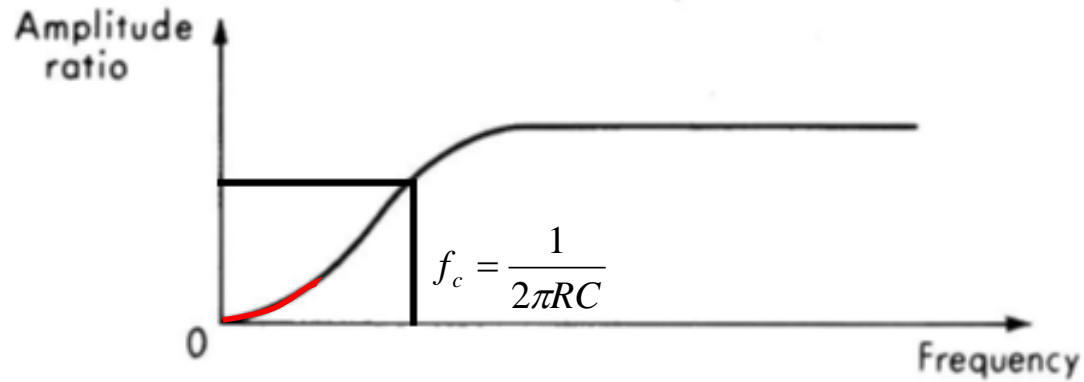
$$G = \frac{v_o}{v_i} = \frac{\frac{\omega}{\omega_c}}{\sqrt{\left(\frac{\omega}{\omega_c}\right)^2 + 1}}$$



High-pass filter

For  $|j\omega CR| \ll 1$  or  $\omega \ll \frac{1}{CR} = \omega_c$

we get  $G = \frac{v_o}{v_i} \cong j\omega CR \ll 1$

or  $v_o(t) = \lambda \cdot j\omega \cdot v_i(t)$  the *output signal* is the “derivative” of the *input signal* !

$\left(\frac{1}{j\omega}\right) \rightarrow$  is an integration operator

$(j\omega) \rightarrow$  is a derivative operator


if we consider, for example, a sinusoidal signal

$v_i(t) = V \sin \omega t = V e^{j\omega t}$  and we *derivate* and *integrate* it :


$$\frac{dv_i(t)}{dt} = \frac{dV e^{j\omega t}}{dt} = j\omega \cdot V e^{j\omega t} = (j\omega) \cdot v_i(t)$$

$$\int v_i(t) dt = \int V e^{j\omega t} dt = \frac{V}{j\omega} \cdot e^{j\omega t} = \left(\frac{1}{j\omega}\right) \cdot v_i(t)$$

# The operational amplifier OA :

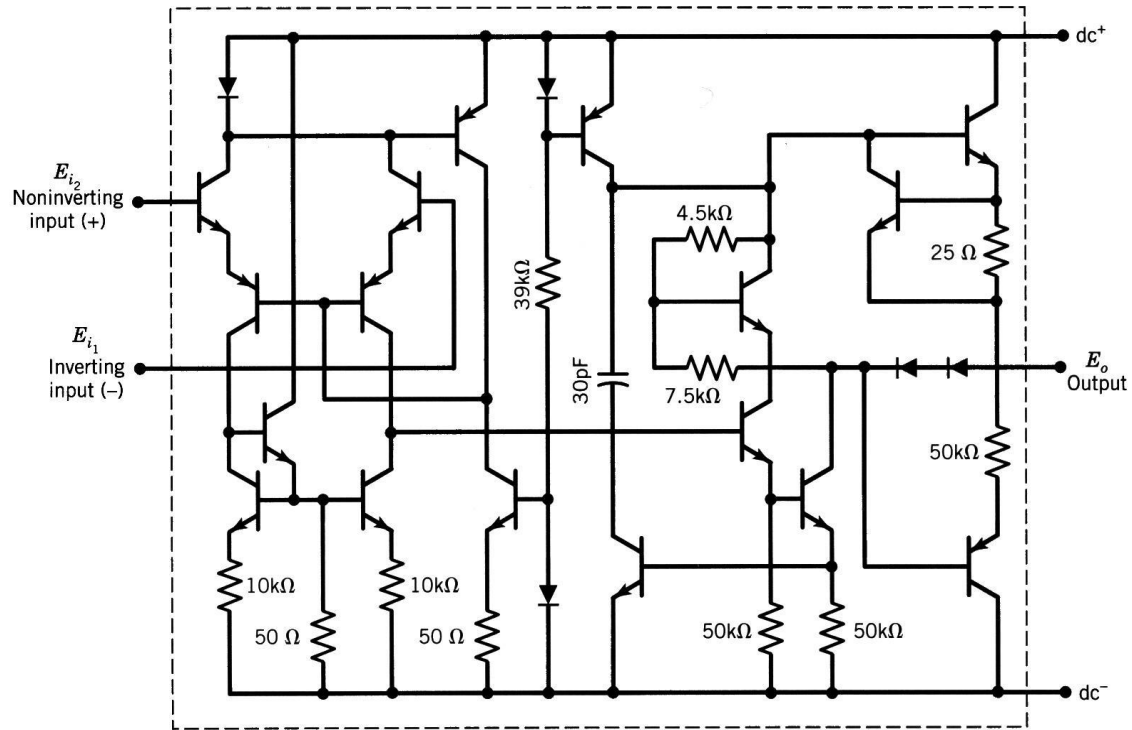



Type 741 circuit diagram

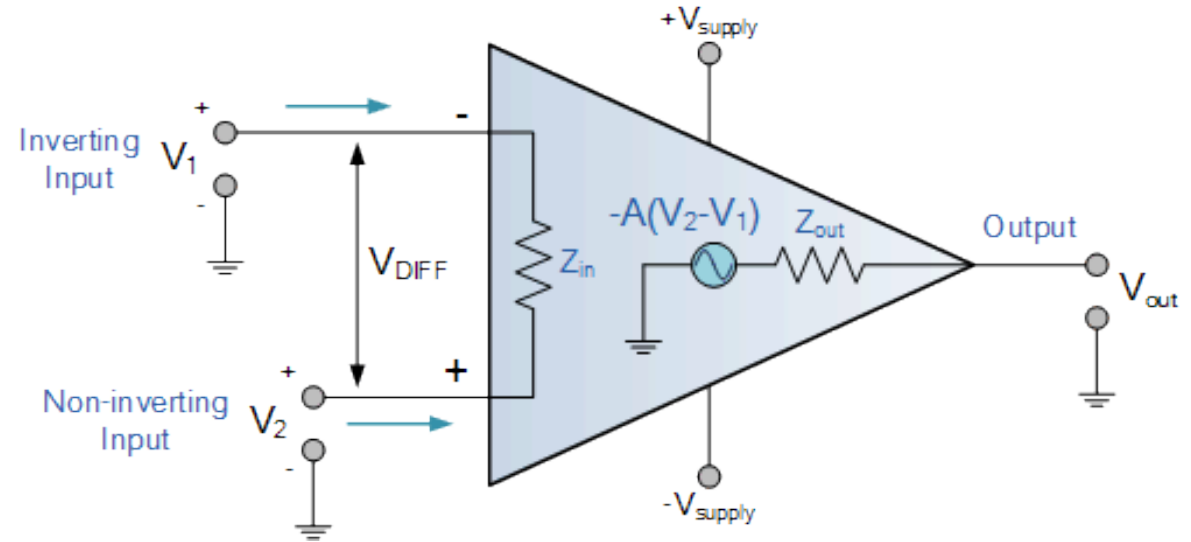

*Ideal* OA characteristics :

Amplification	$A \rightarrow \infty$ ( $10^7$ )
Input impedance	$Z_i \rightarrow \infty$ ( $10^{10} \Omega$ )
Output impedance	$Z_o \rightarrow 0$ ( $100 \Omega$ )
Band width	$BW \rightarrow \infty$
Offset voltage	$V_{io} \rightarrow 0$

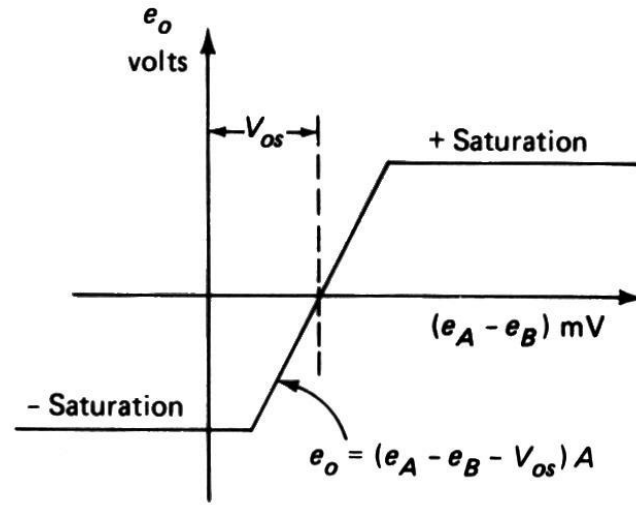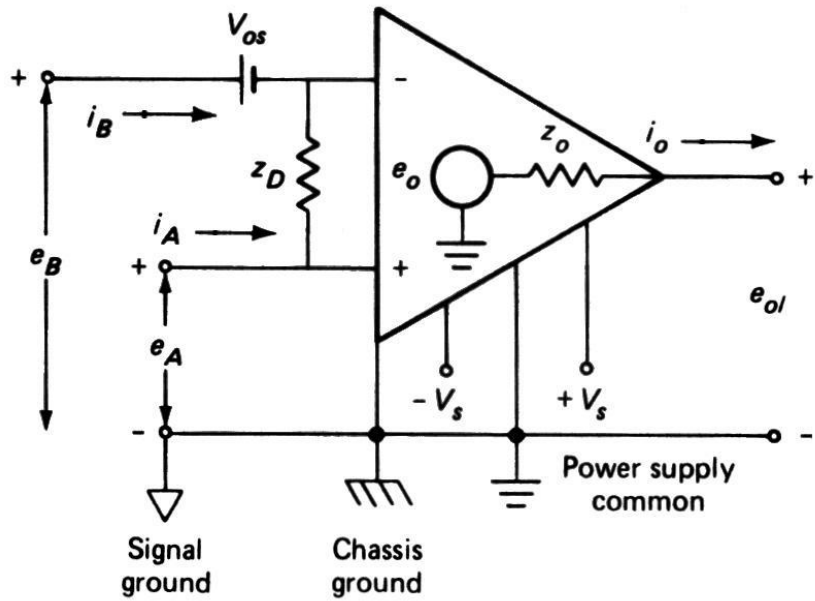We will not study the inner electronic circuits of the OA but the important operational features it offer for the measurements !



The open loop OA can amplify a voltage signal  $V_o = A \cdot (V_+ - V_-)$  but NOT over its supply voltages !


If we have  $V_{cc} = \pm 10V$  and  $A = 10^7$   
Then  $\pm 10V = 10^7 \cdot (V_+ - V_-)_{MAX}$

and  $(V_+ - V_-)_{MAX} = \frac{20V}{10^7} = 2\mu V$  is the

maximum input signal the OA can handle!

The OA goes into saturation for:


$$|V_i| = |V_+ - V_-| > 2\mu V$$

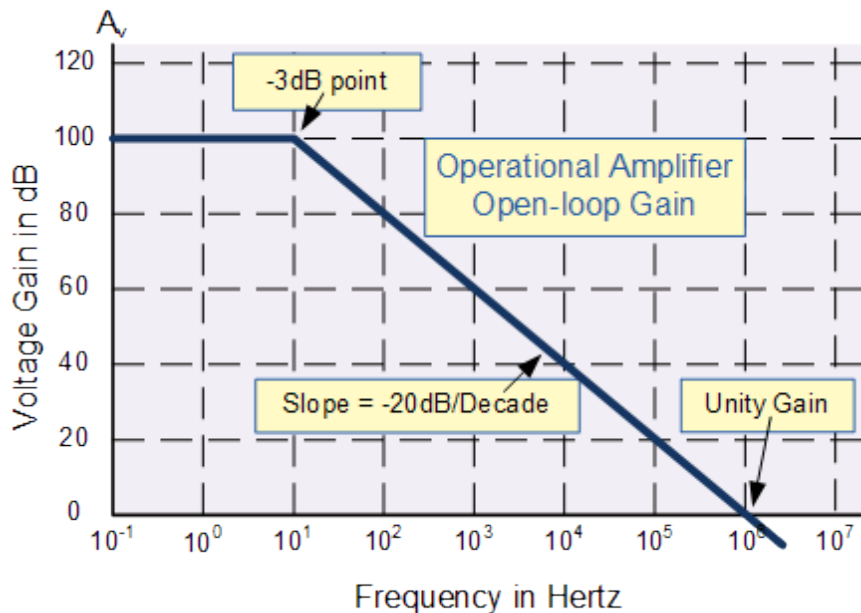

The real *open-loop frequency response* curve is determined by the **Gain Bandwidth Product (GBP)** ...
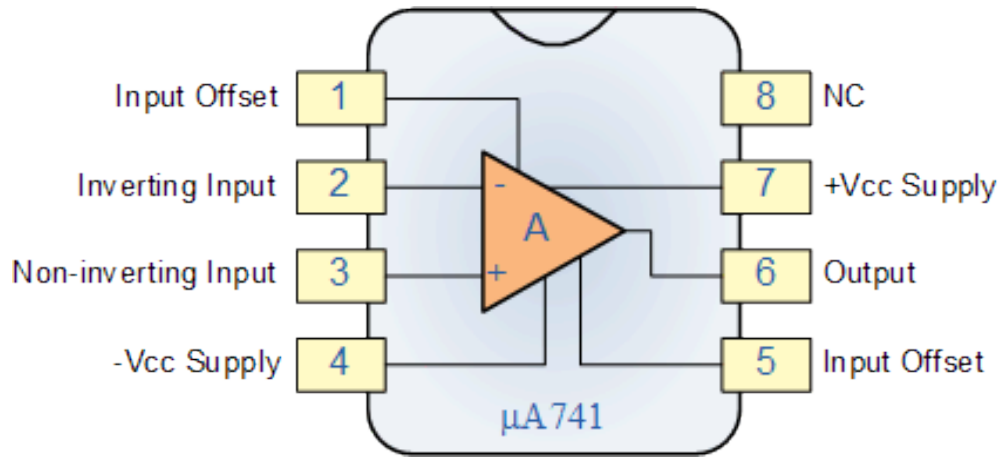
$$20 \log(A) \text{ or } 20 \log \frac{V_{out}}{V_{in}} \text{ in dB}$$





The Operational Amplifier CAN NOT be used as an amplifier in the *open loop configuration* !

Therefore, we must *connect two resistors* at the terminals as showed in the figure, realizing the *inverting operational Amplifier* configuration:

At the virtual earth summing junction we have:

$$V_- \cong V_+ = 0$$

input signal:  $V_i = R_i \cdot i_i$


output signal:  $V_o = R_f \cdot i_f$

The current at the virtual earth point is:  $i_i + i_f = 0$

And because  $i_f = -i_i$  we have

$$V_o = -R_f i_i = -R_f \frac{V_i}{R_i}$$

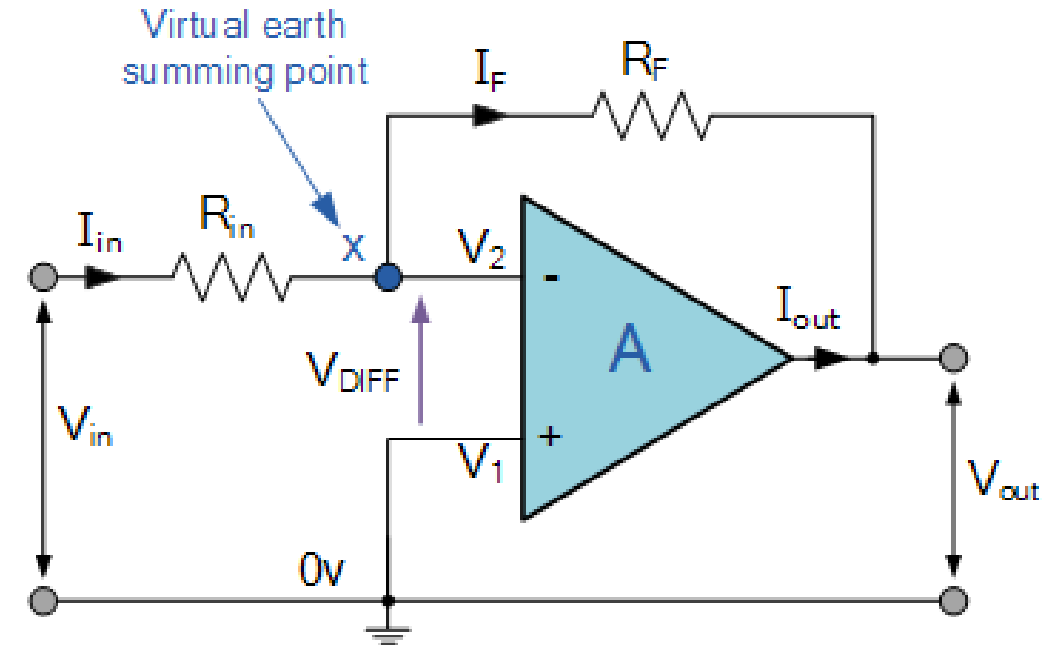
which is the **static characteristic curve** of the device and gives also the **GAIN** of the amplifier:



$$G = \frac{V_o}{V_i} = -\frac{R_f}{R_i}$$

which is **negative** !

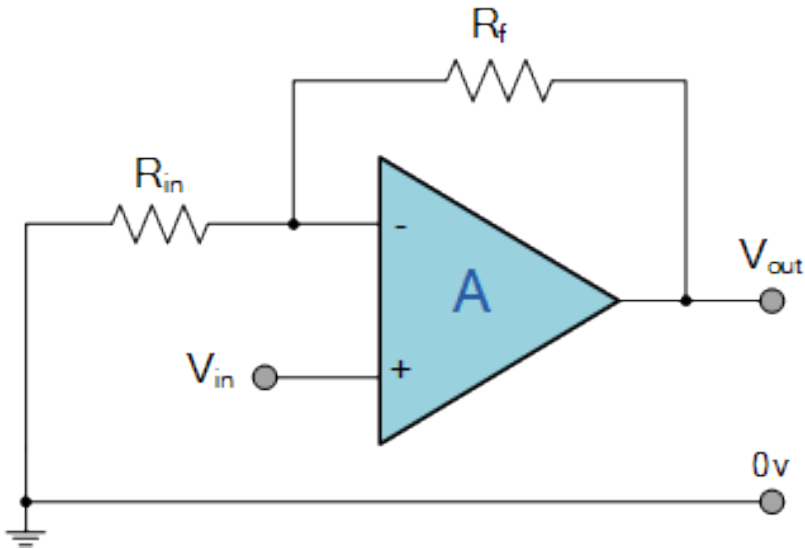To get a “positive” signal amplification we have to switch to the non-inverting operational amplifier configuration:



Because of the “high input impedance” of the OA device, there is *virtually no current* entering the + terminal of the OA and we have now:  $V_- \cong V_+ = V_i$  and  $i_f = i$


So, the output signal can be written as  $V_o = V_f + V_i$  where  $V_f = R_f \cdot i_f$  and  $V_i \cong V_- = R_i \cdot i$

In the end we have:  $V_o = R_f i_f + V_i = R_f i + V_i = R_f \frac{V_i}{R_i} + V_i$

And the **static characteristic curve** now is:

$$V_o = V_i \left( \frac{R_f}{R_i} + 1 \right)$$


with a **positive GAIN** !

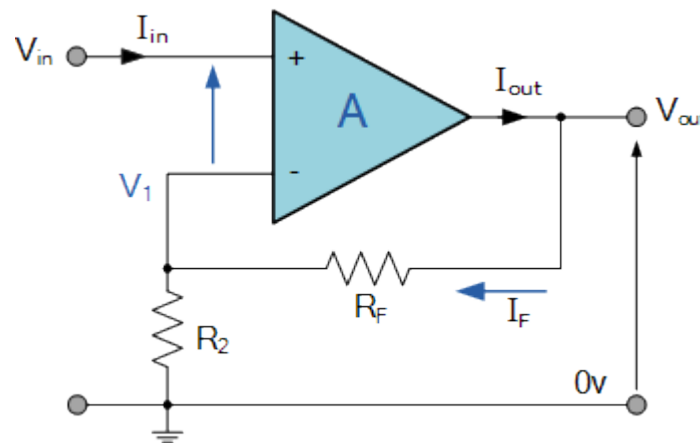

Both configurations have *much lower amplification* than  $10^6 - 10^7$  however the amplification “can be designed” by choosing the two resistance values !

Even if the non-inverting configuration may seem preferable, the inverting configuration has important applications ...

## The voltage summing OA :

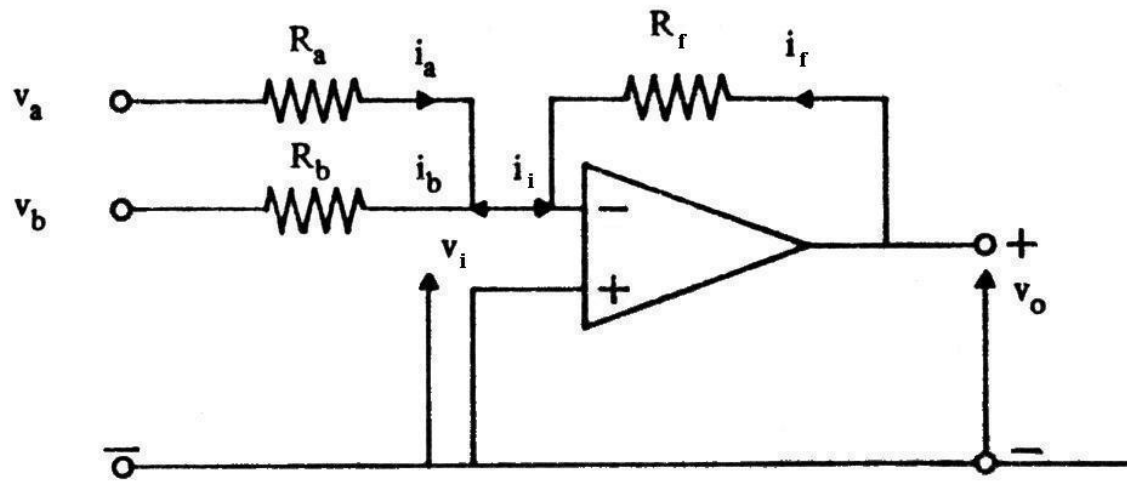

Here we wish to sum two voltages  $V_a$  and  $V_b$

From the inverting OA characteristic curve, we have:

$$V_o = -\frac{R_f}{R_i} V_i = -R_f i_i$$

with 
$$i_i = \frac{V_i}{R_i} = i_a + i_b = \frac{V_a}{R_a} + \frac{V_b}{R_b}$$

If we design the circuit inputs with the two resistance values being equal:  $R_a = R_b = R$


We can simplify the above equation and we obtain :  
***input voltages*** !

$$V_o = -\frac{R_f}{R} (V_a + V_b)$$

which is the ***sum of the two***

Note that summing two voltages means physically to sum the two input currents !
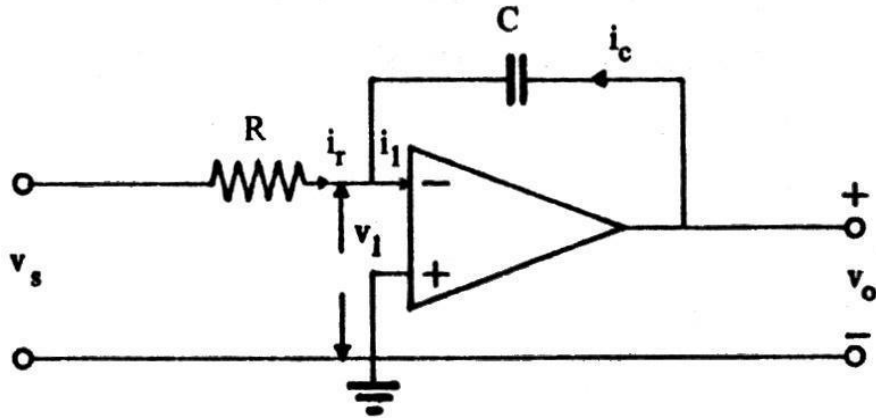
## The active low-pass filter (integrator) :



The gain of the inverting OA is: 
$$v_o = -\frac{Z_f}{Z_i} v_i$$


with  $Z_i = R_i$  and  $Z_f = X_{Cf} = \frac{1}{j\omega C_f}$

Therefore 
$$v_o = -\frac{1/j\omega C_f}{R_i} \cdot v_i = -\frac{1}{j\omega} \cdot \frac{1}{C_f R_i} v_i = -\frac{1}{j\omega} \cdot \omega_c \cdot v_i$$

the *output signal* is the electric integral of the *input signal* !

If we wish to amplify the output, then we have to put an extra resistance  $R_f$  on the feedback arm and the extra gain will be :  $G = R_f/R_i$
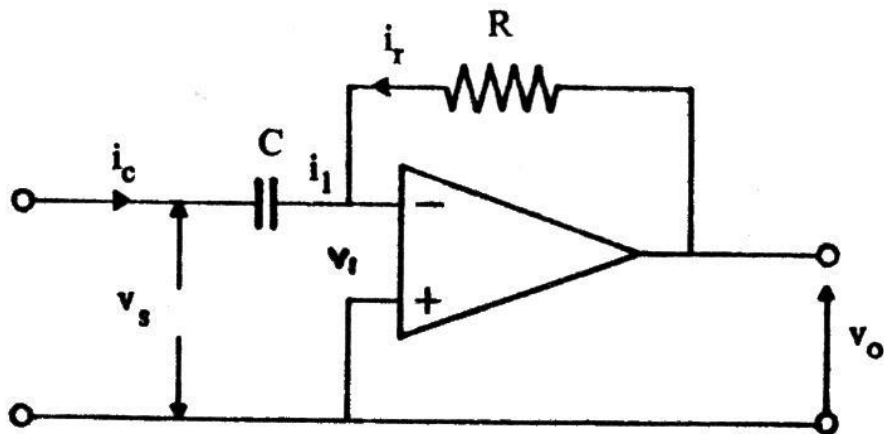
## The active high-pass filter (derivative) :




The gain is still: 
$$v_o = -\frac{Z_f}{Z_i} v_i$$

with  $Z_i = X_{Ci} = \frac{1}{j\omega C_i}$  and  $Z_f = R_f$

so 
$$v_o = -\frac{R_f}{1/j\omega C_i} v_i = -j\omega \cdot C_i R_f \cdot v_i = -j\omega \cdot \frac{1}{\omega_c} \cdot v_i$$

the electric derivative !

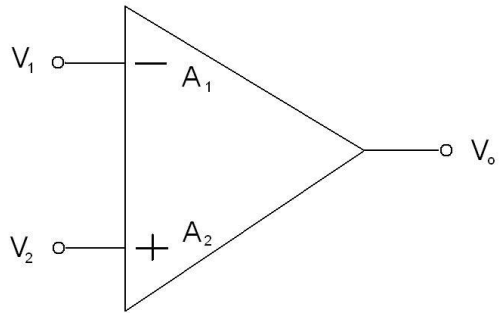

Consider now that the OA accepts TWO voltages at the input terminals  $V_+ = V_2$  and  $V_- = V_1$  both referred to earth, and amplifies its difference:  $V_o = A(V_2 - V_1)$  ... But this is true in the IDEAL case !  
 In the reality, there are TWO slightly different amplifications at the inputs:  
 $V_o = A_2V_2 - A_1V_1$  ...

This situation can be effectively described by the **differential input**:  $V_d = V_2 - V_1$  and the **common mode input**:  $V_c = \frac{V_1 + V_2}{2}$  which is the mean distance from the earth reference of the two input voltages.

For an ideal OA we would have  $A_1 = A_2 = A$  and the OA would amplify only the differential input, completely eliminating the common mode input !


This situation can be effectively described by the **differential amplification**:  $A_d = \frac{A_1 + A_2}{2}$  which operates on  $V_d$  and by the **common mode amplification**:  $A_c = A_2 - A_1$  which operates on  $V_c$   
 To minimize this problem the OA must be designed with a high  $A_d$  and a very small  $A_c$  which means  $A_1 \approx A_2$

The ratio between the two amplifications is an important quality parameter of the OA, the **Common Mode Rejection Ratio**:  $CMRR = \frac{A_d}{A_c}$  often expressed in logarithmic scale

Values range from 60 dB up to 120 Db for high quality OA ...

$$CMRR = 20 \log \frac{A_d}{A_c}$$

## The Instrumentation Amplifier IA :

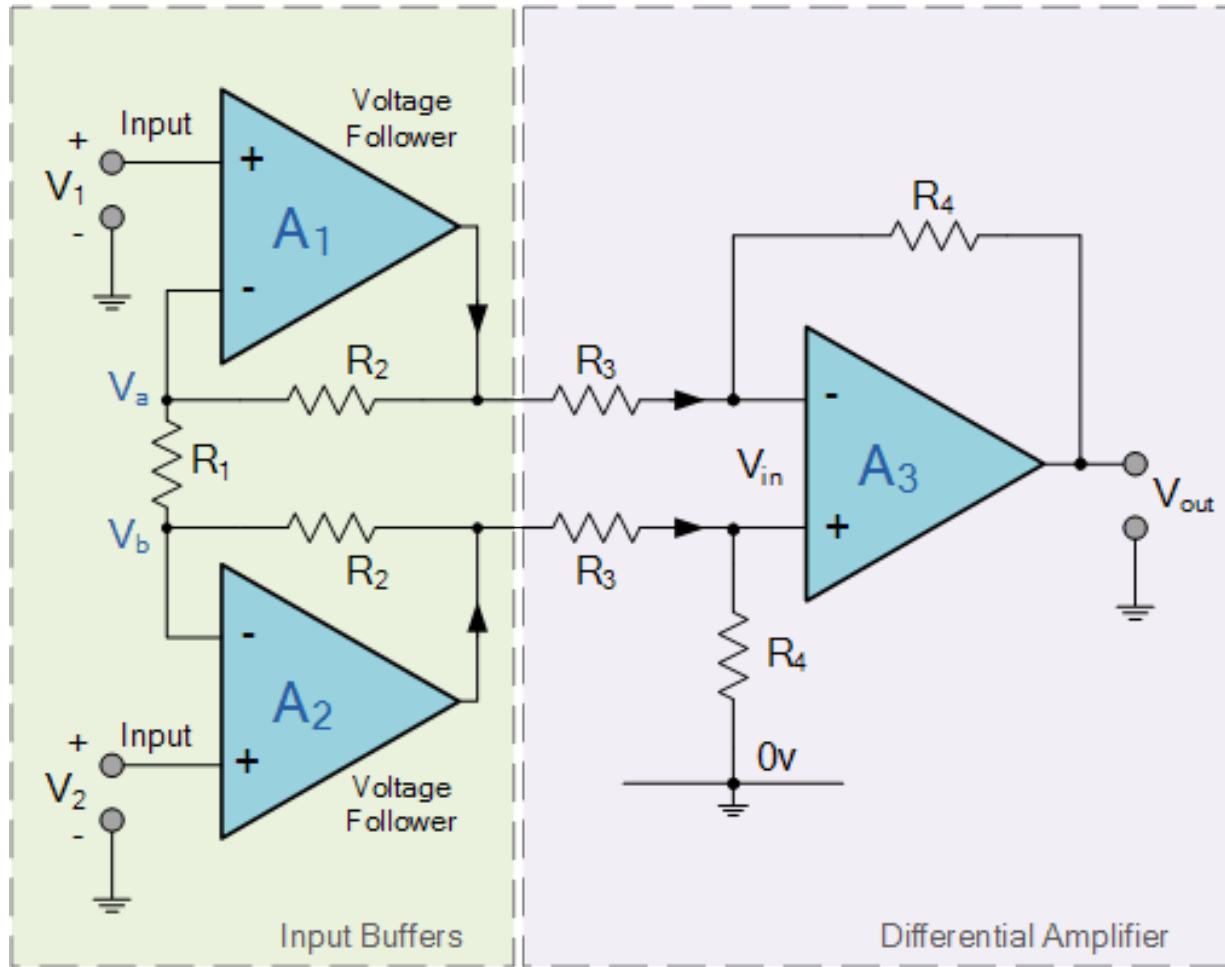

The most employed amplifier in measurements is designed with two stages:

1. A very high input impedance stage ( $10^{10} \Omega$ )
2. A differential amplification stage


It has generally a very high **Common Mode Rejection Ratio** ( $> 100 \text{ dB}$ ) which makes it suitable to amplify *floating signals* ( $v_2 - v_1$ ) ...

The (differential) **GAIN** is :

$$G = \frac{v_o}{v_i} = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right)$$



# The Carrier AC Amplifier :

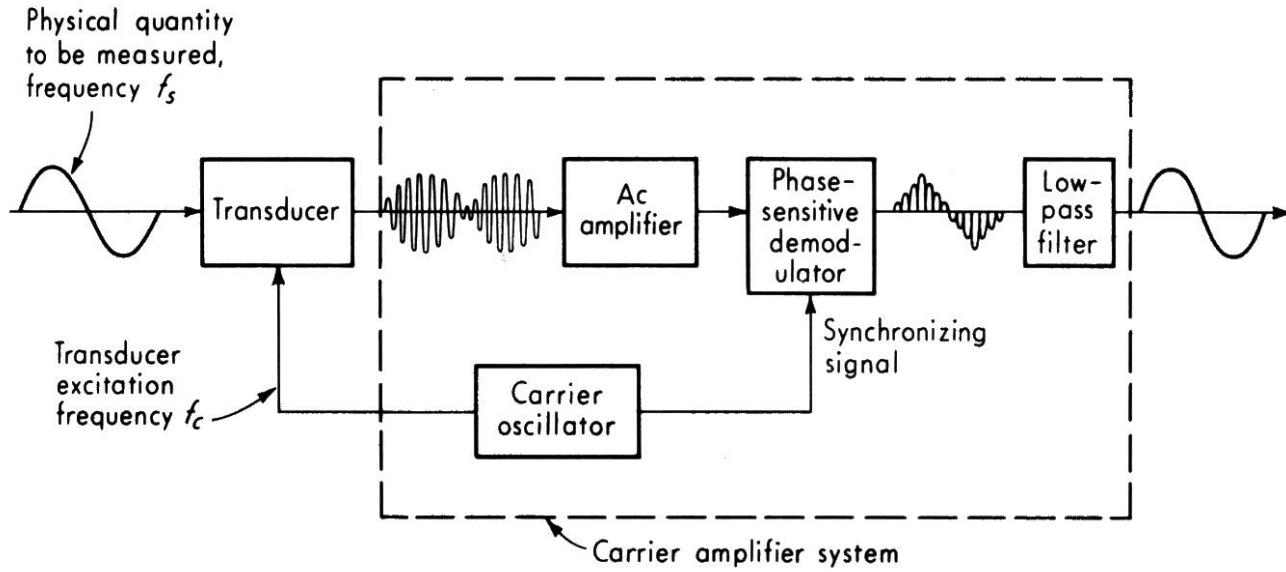


The **Carrier Amplifier** is an AC amplifier which does NOT amplify DC signals or components !

It is designed on the “signal modulation and demodulation” principle of radio transmission !


The low frequency ( $f_s$ ) signal is modulated by the carrier frequency ( $f_c$ ) which is the only frequency the amplifier is able to amplify !

A *phase sensitive demodulator* and a *low pass-filter* return an amplified low frequency signal !


## Modulation

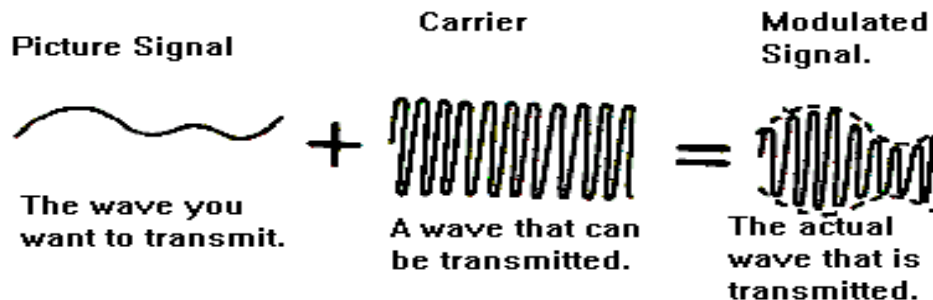

## Demodulation

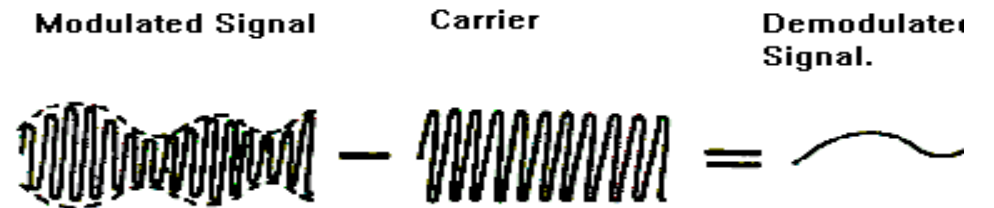

## The Wheatstone Bridge :

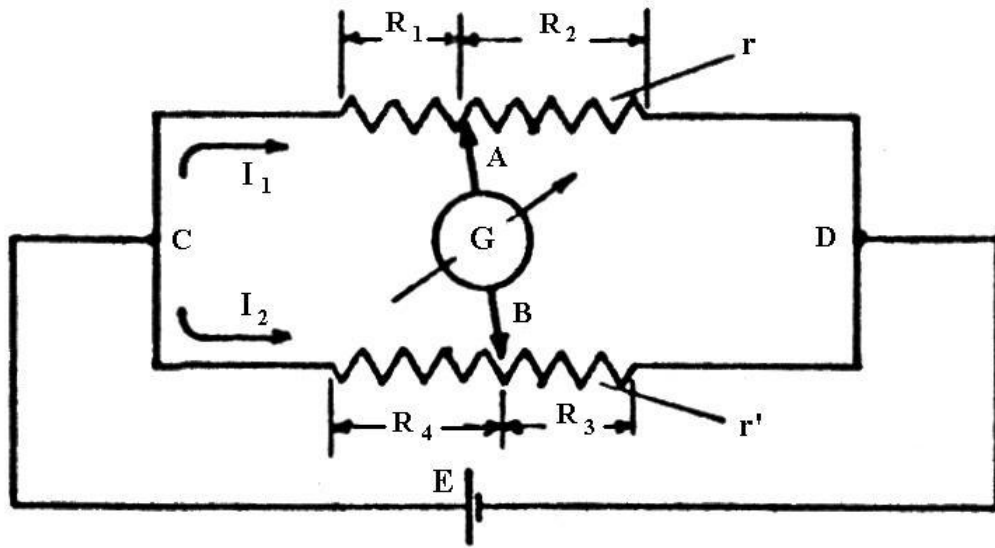

Two resistances  $r$  and  $r'$  are connected in parallel and a *galvanometer*  $G$  is connected in a bridge configuration across the two resistances in the points  $A$  and  $B$  ...

We move now the point  $A$  and  $B$  on the resistances so to have zero current though the galvanometer, which means also:  $V_A = V_B$


In this situation we identified 4 resistances :  $R_1, R_2, R_3, R_4$  for which we can write the following equations:

$$V_{CA} = V_{CB} \quad \rightarrow \quad R_1 I_1 = R_4 I_2$$

$$V_{AD} = V_{BD} \quad \rightarrow \quad R_2 I_1 = R_3 I_2$$

Making the ratio of the two equations, we get:  $\frac{R_1}{R_2} = \frac{R_4}{R_3}$  or  $\boxed{R_1 R_3 = R_2 R_4}$  the bridge equilibrium equation !

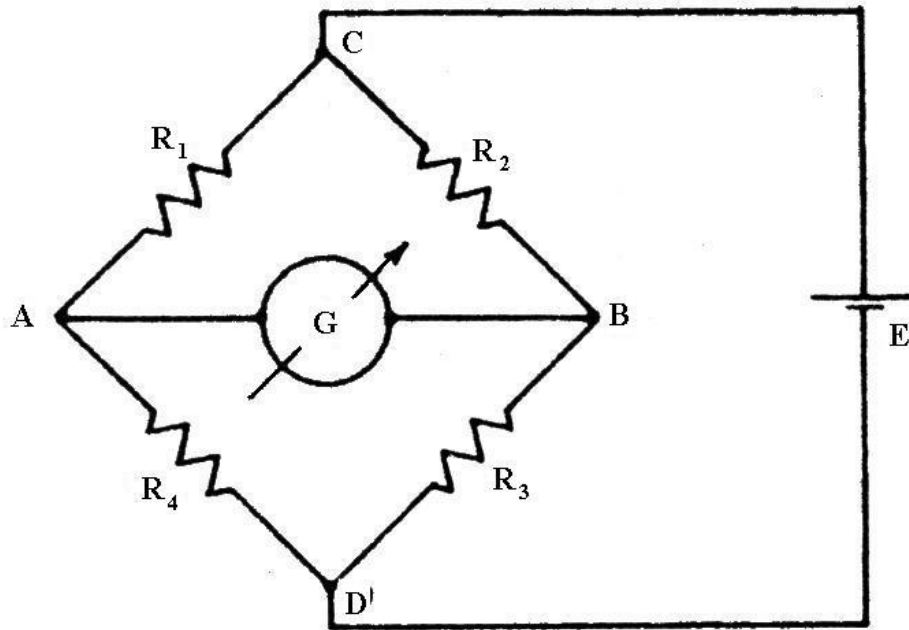No current through the bridge means also  $V_A - V_B = 0$  therefore, in practical application, we can substitute the *galvanometer* with a *millivoltmeter* !



The **Wheatstone Bridge** is a “zero method” electric network used for resistance measurements:

If  $R_x = R_1$  is unknown, we equilibrate the bridge by operating on  $R_2$  and, knowing the values of  $R_2, R_3, R_4$ , we get:

$$R_x = R_1 = \frac{R_2 R_4}{R_3}$$

However, this is NOT the main use of the Wheatstone Bridge ...

We might have a resistance  $R_1$  that changes slightly its value  $\Delta R_1$  for physical reasons ...


It is possible to read this small change directly on the voltmeter indicator but, to do so, we need to know the ***bridge graduation curve*** (or *static characteristic equation*):  $V_{AB} = f(\Delta R_1)$

If we consider for simplicity a bridge with 4 equal resistances:  $R_1 = R_2 = R_3 = R_4 = R$  and a variation  $\Delta R_1$  only on the resistance  $R_1$ , we get:

The complete **Wheatstone Bridge characteristic curve** :

$$\frac{\Delta e}{E} = \frac{\frac{1}{4} \cdot \frac{\Delta R_1}{R}}{1 + \frac{1}{2} \cdot \frac{\Delta R_1}{R}}$$

which is clearly **NON linear** !

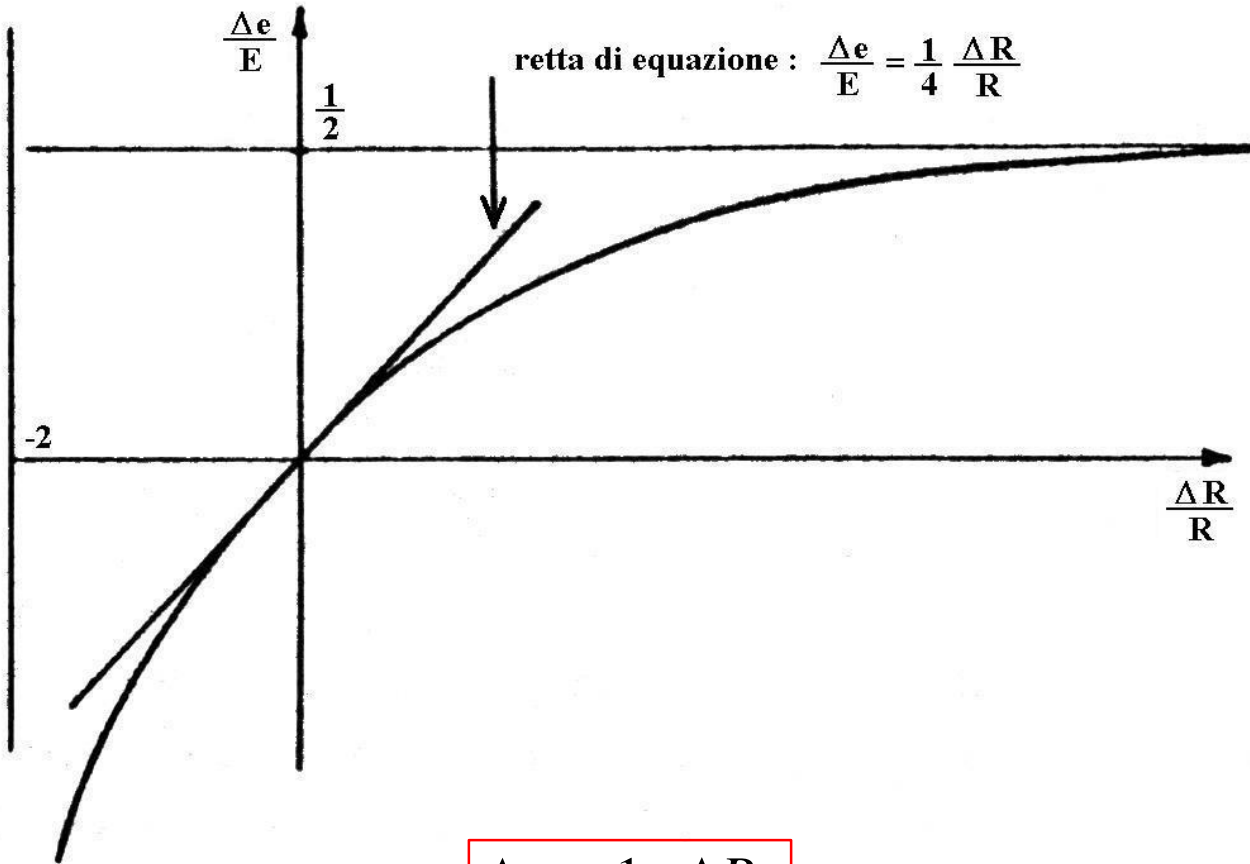

However, if the variation  $\Delta R_1 \ll R$  is

really **very small**:  $\frac{\Delta R_1}{R} < 0.01$

Then, the denominator of the graduation curve can be approximated with "1"

$$\frac{1}{2} \frac{\Delta R_1}{R} \ll 1$$

and the *characteristic equation has been linearized* !

$$\frac{\Delta e}{E} \approx \frac{1}{4} \cdot \frac{\Delta R_1}{R}$$

**Linearized Wheatstone Bridge characteristic curve** !

Same result if the only resistance with a small variation  $\Delta R_2$  would have been  $R_2$  on the second arm of the bridge:

$$\frac{\Delta e}{E} \cong -\frac{1}{4} \cdot \frac{\Delta R_2}{R}$$

negative because  $R_2$  is in the negative term of the equilibrium equation:  $R_1 R_3 - R_2 R_4 = 0$

In the case of simultaneous small variations of all 4 resistances of the Wheatstone Bridge , we would get:

$$\frac{\Delta e}{E} = \frac{1}{4} \left( \frac{\Delta R_1}{R} - \frac{\Delta R_2}{R} + \frac{\Delta R_3}{R} - \frac{\Delta R_4}{R} \right)$$

The ***Full Wheatstone Bridge characteristic curve*** ! ( note the sign alternations ... very important property ...)